


INSTRUCTION

EXPERIMENTAL TABLE

Resistance: 6 K Ω

Serial No.	Voltage(Volt) V	Current(milliAmpere) mA
1	1	0.167
2	3	0.500
3	6	1.00
4	11	1.83
5	17	2.83
6	19	3.17

Ohm's Law

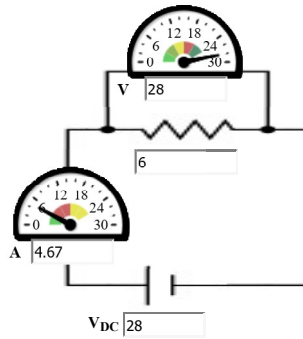

CONTROLS


DC volt : Volt
Resistance : Kohms

Add to Table

Plot

Clear

GRAPH PLOT

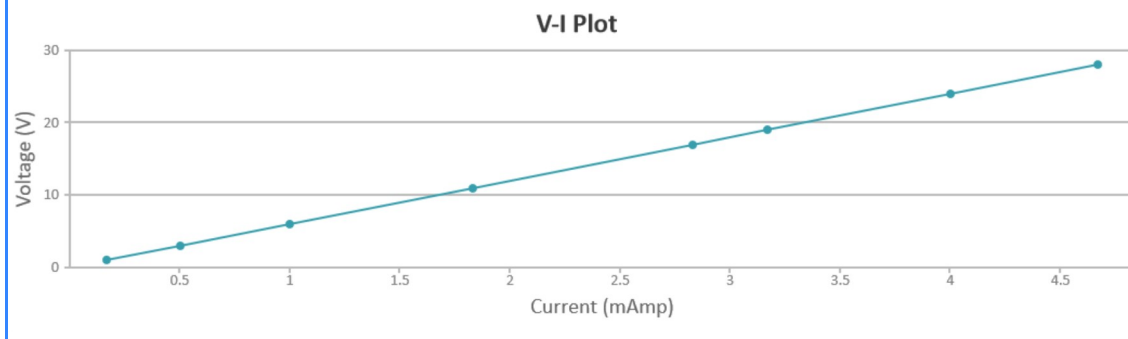Copyright © 2011 Indian Institute of
Technology Kharagpur, [Licensing Terms](#)